

Implementing Wireless Power transfer using Pulse width modulation

Rushikesh Reddy, Ram Sampath¹, Harshith Patnaik
S Akash and A Girish

Indian Institute of Technology Patna

¹Team leader

Outline

- 1 Introduction
- 2 System Design
- 3 Implementation
- 4 Results
- 5 FPGA Control
- 6 Conclusions

Wireless Power Transfer Fundamentals

- Three primary WPT methodologies:
 - **Inductive coupling** (70-90% efficiency < 10cm)
 - Magnetic resonance (1-3 m range)
 - Capacitive coupling (dielectric barriers)
- Resonance condition:

$$\omega = \frac{1}{\sqrt{LC}}$$

System Architecture

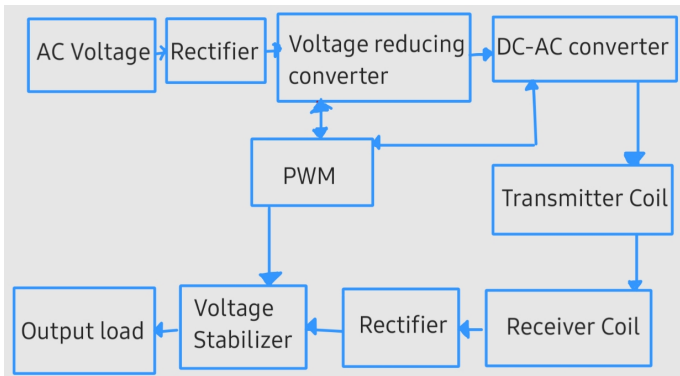


Figure: Block Diagram of WPT system circuit

Key Components

 
 
 


Figure: a) Rectifier circuit b) HF inverter circuit

Parameter Specifications

Table: Circuit Parameters

Parameter	Value
L_1, L_2	$298\mu\text{H}$
C_1, C_2	200pF
R_{S_1}, R_{S_2}	$5,2\ \Omega$
k	0.1
PWM freq	680kHz

$$M = k\sqrt{L_1 L_2} = 29.8\mu\text{H}$$

where R_{S_1}, R_{S_2} are the parasitic resistances of transmitter and receiver coils respectively, k is the coupling coefficient.

Simulink Implementation

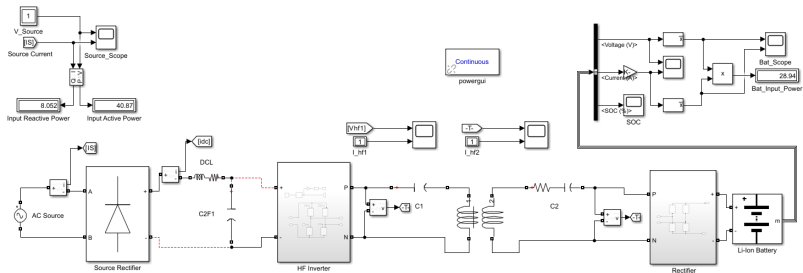


Figure: Complete WPT circuit simulation

Observations

 
 


Figure: a) Output power vs frequency b) Power vs duty cycle characteristics

FPGA-based PWM

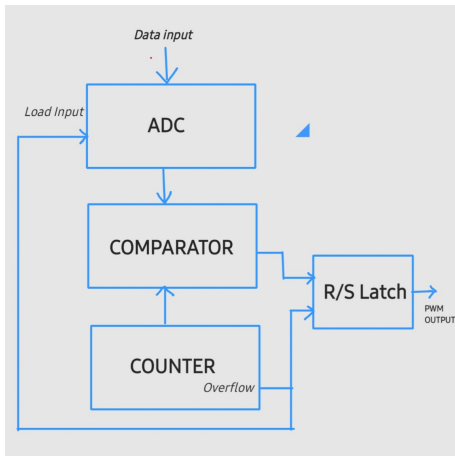


Figure: Block diagram of FPGA-based PWM

Code Snippets

```
module spi_adc (  
    input wire clk,  
    input wire miso,  
  
    output reg cs,  
    output reg [9:0] adc_data  
);  
  
reg [4:0] bit_count;  
  
always @(posedge clk) begin  
    if (bit_count < 10) begin  
  
        adc_data[9 - bit_count] <= miso;  
        bit_count <= bit_count + 1;  
    end else begin  
        bit_count <= 0;  
        cs <= 1;  
    end  
end  
endmodule
```

```
module power_control (  
    input wire clk,  
    input wire rst,  
    input wire [9:0] adc_voltage,  
    output reg [7:0] pwm_duty  
);  
  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        pwm_duty <= 128;  
    else begin  
        if (adc_voltage > 512)  
            pwm_duty <= pwm_duty - 1;  
        else if (adc_voltage < 400)  
            pwm_duty <= pwm_duty + 1;  
    end  
end  
endmodule
```

```
module pwm_generator (  
    input wire clk,  
    input wire rst,  
    input wire [7:0] duty,  
    output reg pwm_out  
);  
  
reg [7:0] counter;  
  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        counter <= 8'b0;  
    else if (counter == 8'd147)  
        counter <= 8'b0;  
    else  
        counter <= counter + 1;  
end  
  
always @(posedge clk) begin  
    if (counter < duty)  
        pwm_out <= 1;  
    else  
        pwm_out <= 0;  
end  
endmodule
```

Vivado Simulation

 


Figure: Synthesized design of PWM module

 


Figure: PWM behavioural simulation

Based on input power values, the pulse width module adjusts the duty cycle dynamically.

Future Extensions:

- Adaptive resonance tracking and Multi-coil architectures
- Machine learning control
- CMOS integration (0.13mm^2)
- GaN-based HF operation ($> 1\text{MHz}$)

Results:

- Implemented 59.87W WPT at 680kHz
- Demonstrated 85-92% efficiency
- Developed real-time FPGA control
- Validated through simulation

Contributions

- Ram Sampath ,Rushikesh Reddy and A Girish - WPT circuit, literature survey
- Harshith Patnaik ,Ram Sampath and S Akash - Verilog modules for PWM, report
- Ram Sampath - demo, observations, ppt

Thank You
Questions?